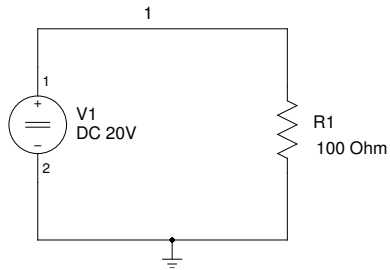


Name: _____

(no class)
(no term)
(testing image example)

This test shows how a problem can include an image.

1. Calculate the current through the voltage source and the resistor.



Solution: 200 mA